

8-bit Breadboard Computer

Introduction

The intention is that this document will serve as a reference manual, with enough detail to fully refresh the concepts that govern the operation of the CPU, while avoiding being a tome that covers every detail from the YouTube videos.

1 Clock Module

The clock module permits variable speeds, as well as single clock pulses using a push-button. This section will cover all iterations of the timer: *astable*, *bistable*, and *monostable*.

1.1 Astable 555 Timer

In this configuration, the 555 timer is simply used with two resistors and a capacitor to set the time the output will be off and on. Figure 1 shows the circuit diagram and voltage across the capacitor.

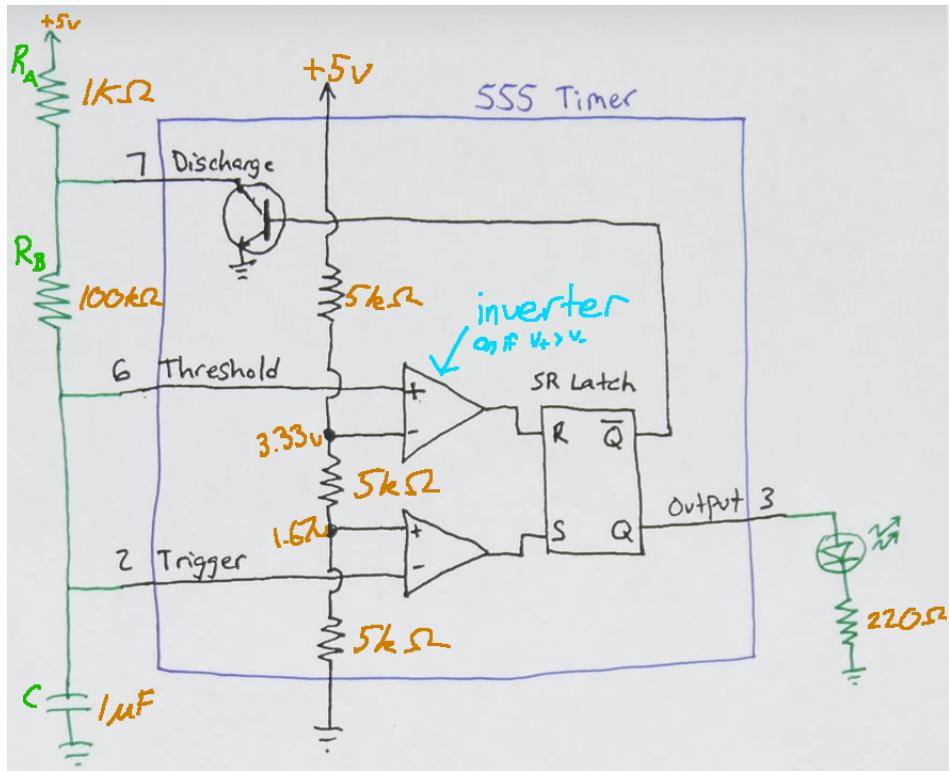


Figure 1: Astable 555 Timer Circuit Diagram

The datasheet provides some equations for determining the charge time (Equation 1), discharge time (Equation 2), total period (Equation 3), and frequency of oscillation (Equation 4).

$$t_1 = 0.693(R_A + R_B)C \quad (1)$$

$$t_2 = 0.693(R_B)C \quad (2)$$

$$T = t_1 + t_2 = 0.693(R_A + 2R_B)C \quad (3)$$

$$f = \frac{1}{T} = \frac{1.44}{(R_A + 2R_B)C} \quad (4)$$

The completed circuit is shown in Figure 2. Before the last few capacitors were added to the circuit, the oscilloscope probes were hooked to the positive lead of the capacitor, as well as the output of the SR latch. This data is shown in Figure 3. Note: the values on both scales of the oscilloscope data are not accurate, it's the shape that's important.

Of particular note in Figure 3 is the overshoot on the output of the SR latch. This is largely caused by the impedance and inductance in the relatively long power cable, as it causes a delay in the time for the power supply to supply enough power to turn the LED on (and do the other thing that happen inside the 555 chip). This can be remedied by placing a $0.1\mu F$ capacitor across the power lines of the breadboard. Similarly, the datasheet recommends placing a $0.01\mu F$ capacitor from pin 5 to GND, to reduce noise. A plot of this data is not included as it does not show up very clearly on a cheap oscilloscope.

Finally, note that the $100K\Omega$ resistor in Figure 1 has been replaced by a variable resistor (0 to $1M\Omega$) in Figure 2, so that the clock speed can be varied.

Some text

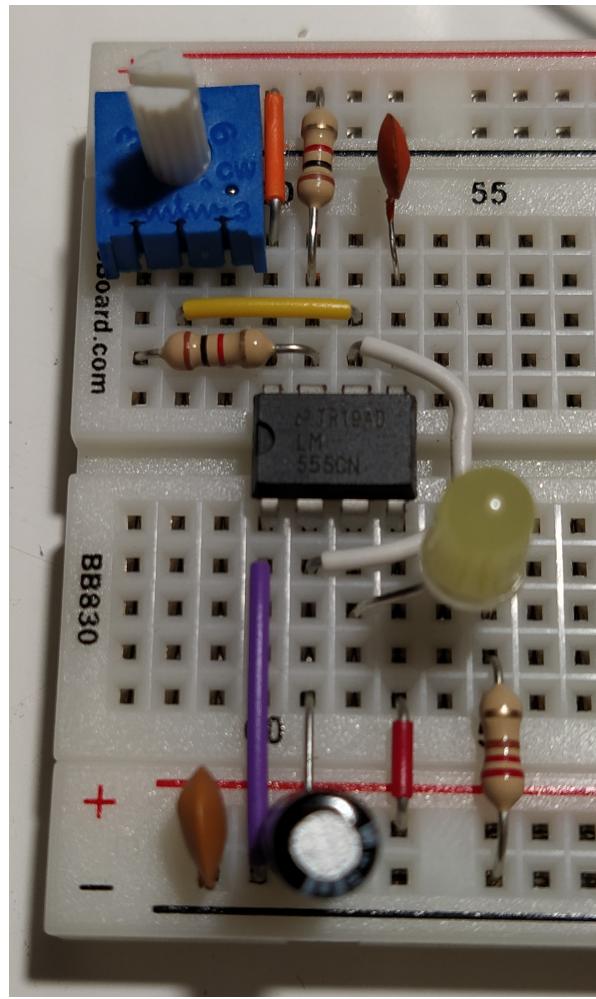


Figure 2: Astable 555 Timer Circuit

Time	Capacitor Voltage	S	R	Q	\bar{Q}	Transistor	
t_0	0		1	0	1	0	Off
t_1	> 1.67		0	0	1	0	Off
t_2	> 3.33		0	1	0	1	On
t_3	< 3.33		0	0	0	1	On
t_4	< 1.67		1	0	1	0	Off

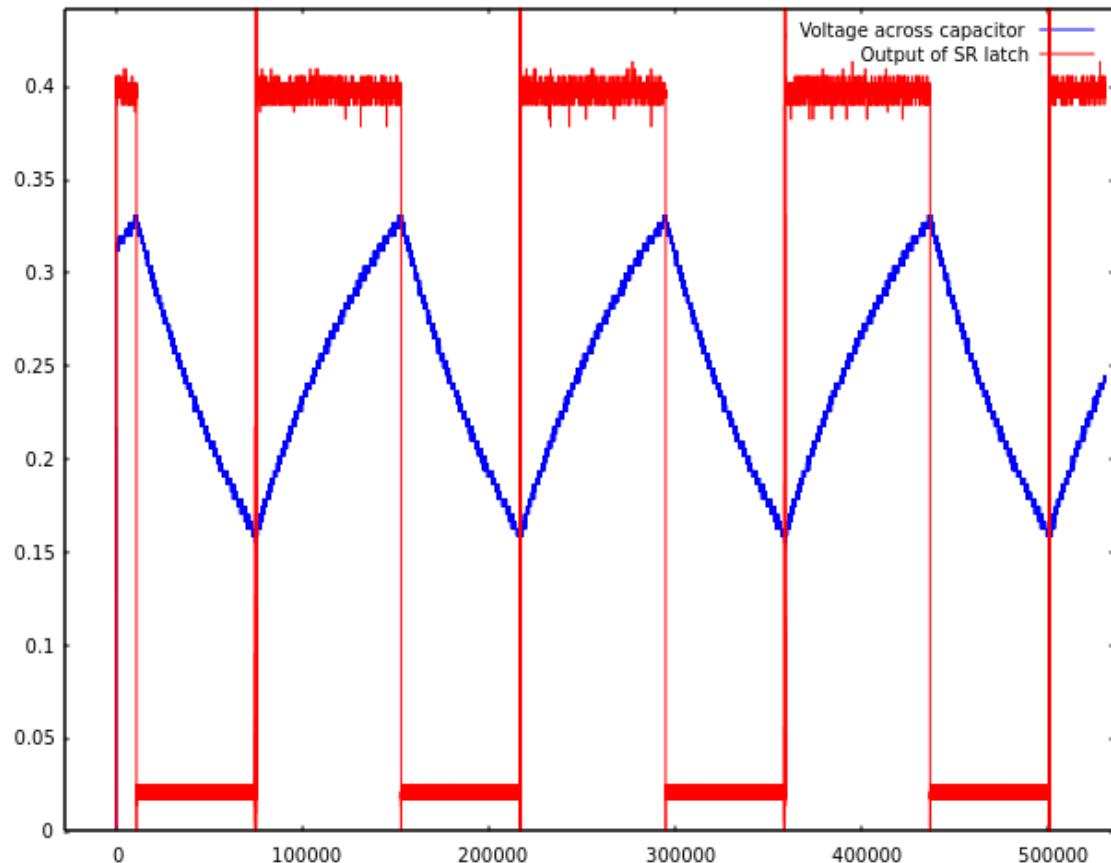


Figure 3: Astable 555 Timer Oscilloscope Data

1.2 Monostable 555 Timer

To allow us to manually advance the clock by one clock cycle, we will use a 555 timer to debounce a pushbutton. Appro